

Laboratory Report # 1

Name: Machacon, Zach Riane I. Date Completed: September 1, 2023

Laboratory Exercise Title: Design Flow of Digital Systems

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 1C:

 


Figure 1: Project Settings Summary of HalfAdder

The project made use of DE-10 Lite board with an Intel Max 10 10M50DAF484C7G FPGA.



```
◍
                                                                                       ×
                                         HalfAdder.v
 4
    Machacon, Zach Riane I.
 2
          CPE 3101L (Group 2) F 11:00AM - 2:00PM
 3
          Verilog HDL code for a half adder circuit
 4
5
       module HalfAdder (x, y, C, S);
 6
7
                   x, y;
c, s;
          input
                   c, s;
X1 (s, x, y);
A1 (c, x, y);
 8
          output
 9
          xor
10
          and
11
12
       endmodule
```

Figure 2: Design Entry for HalfAdder in Verilog HDL

As indicated by the code, there will be 2 inputs and 2 outputs, along with the use of 1 XOR and 1 AND gate.

 


Figure 3: Compilation Report for the Flow Summary of HalfAdder

According to the compilation report, 2 logic elements and 4 total pins are needed. Quartus also found 1 warning, however, it is negligible and does not interfere with the synthesis process.



 


Figure 4: Schematic Diagram of Synthesized Circuit from HalfAdder Project

As expected, a half adder circuit was constructed from the design entry. 2 inputs, x and y, are put into both the XOR and AND gates. The result of the AND gate is the CARRY, and the result of the XOR gate is the SUM.