



Laboratory Report # 3

Name: Machacon, Zach Riane

Date Completed: September 22, 2023

Laboratory Exercise Title: Structural Modeling of Combinational Circuits

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 3A:

Solution:

Truth Table for 2x4 Decoder

E	A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Boolean Expressions:

$$D_3 = A_1 A_0 E \quad D_0 = A_1' A_0' E$$

$$D_2 = A_1 A_0' E$$

$$D_1 = A_1 A_0' E$$

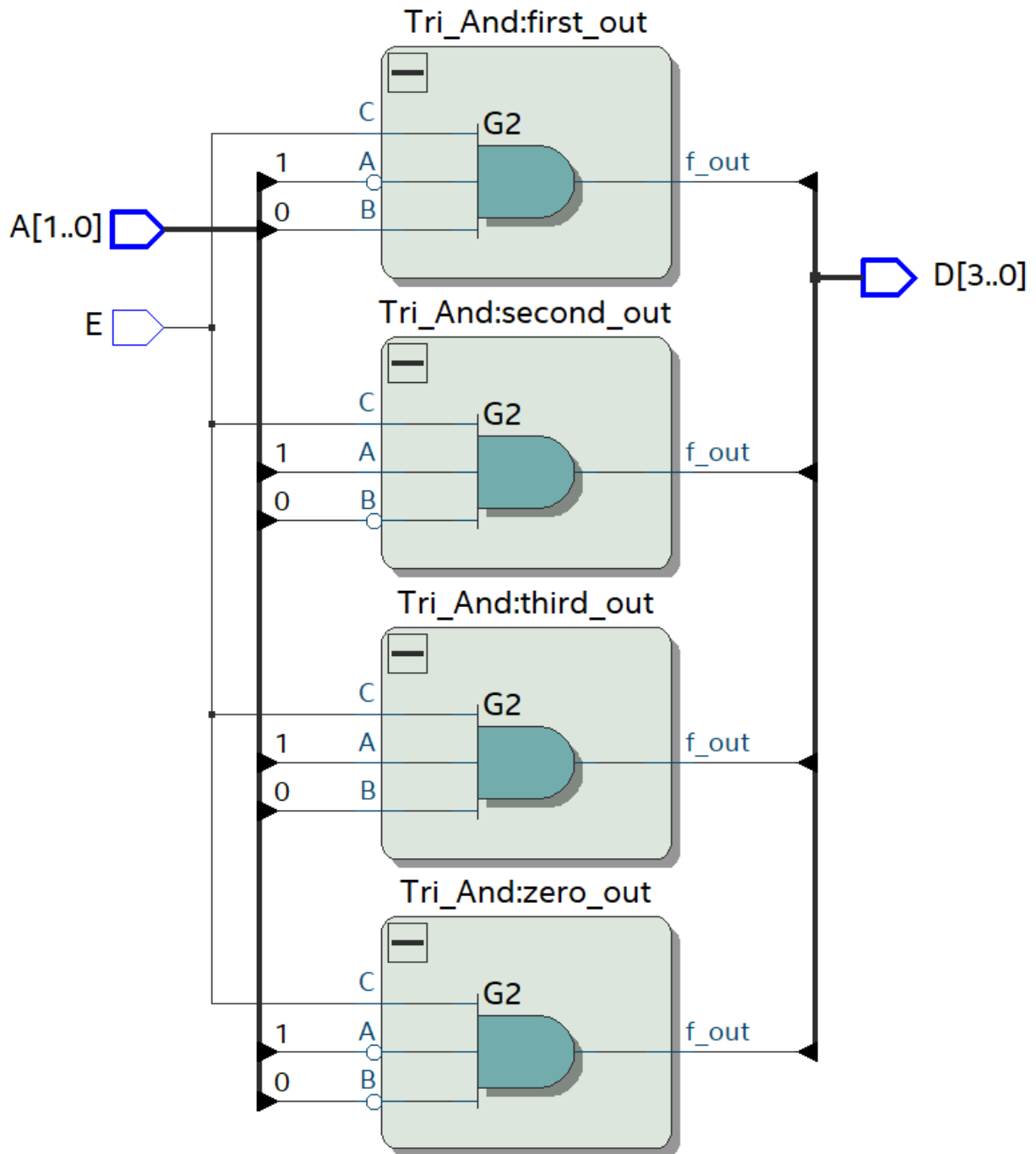


Figure 1: Logic Diagram with Labels of Decoder_2x4

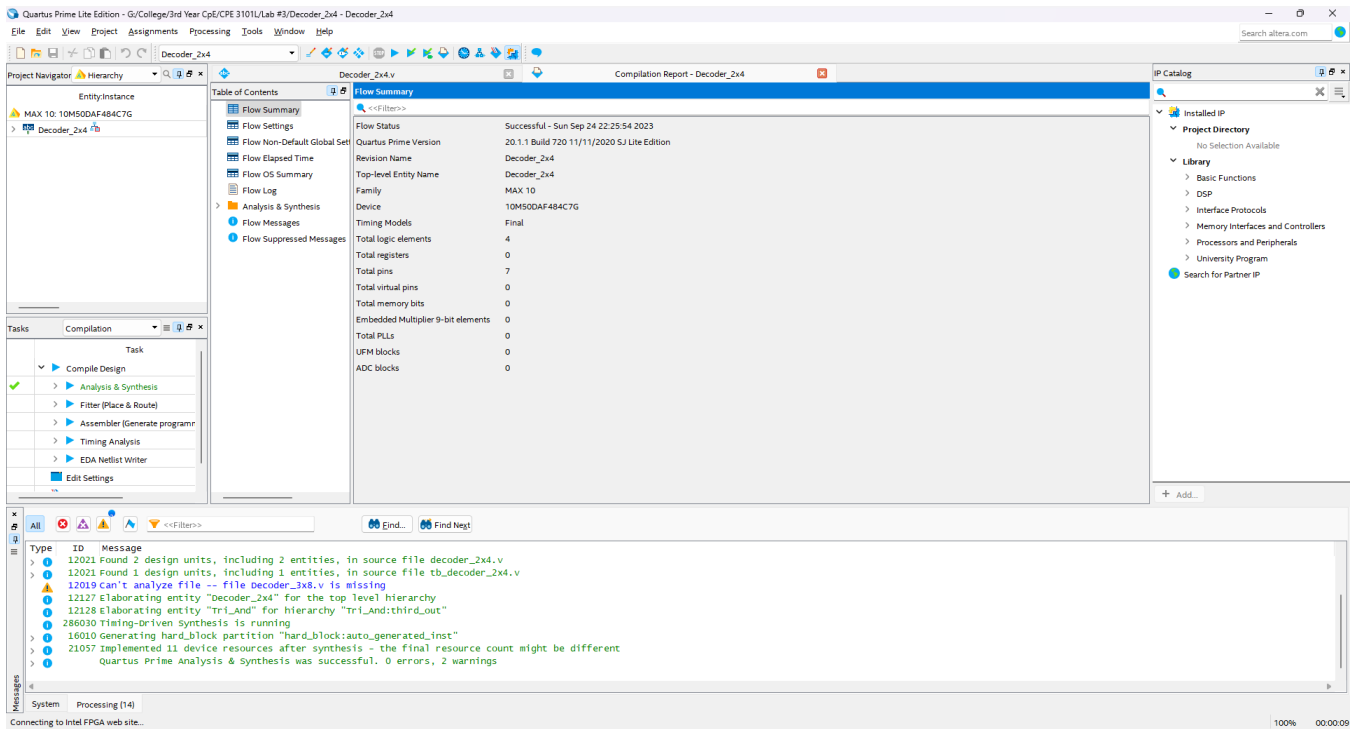


Figure 2: Successful Design Synthesis of Decoder_2x4

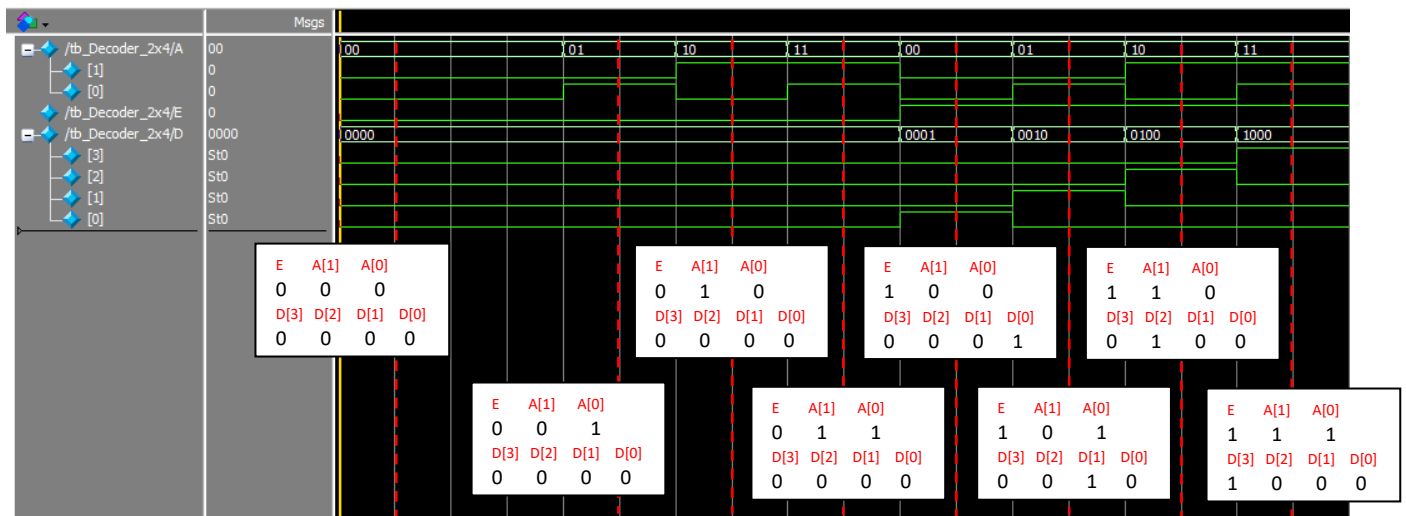


Figure 3: Successful Simulation Results of Decoder_2x4

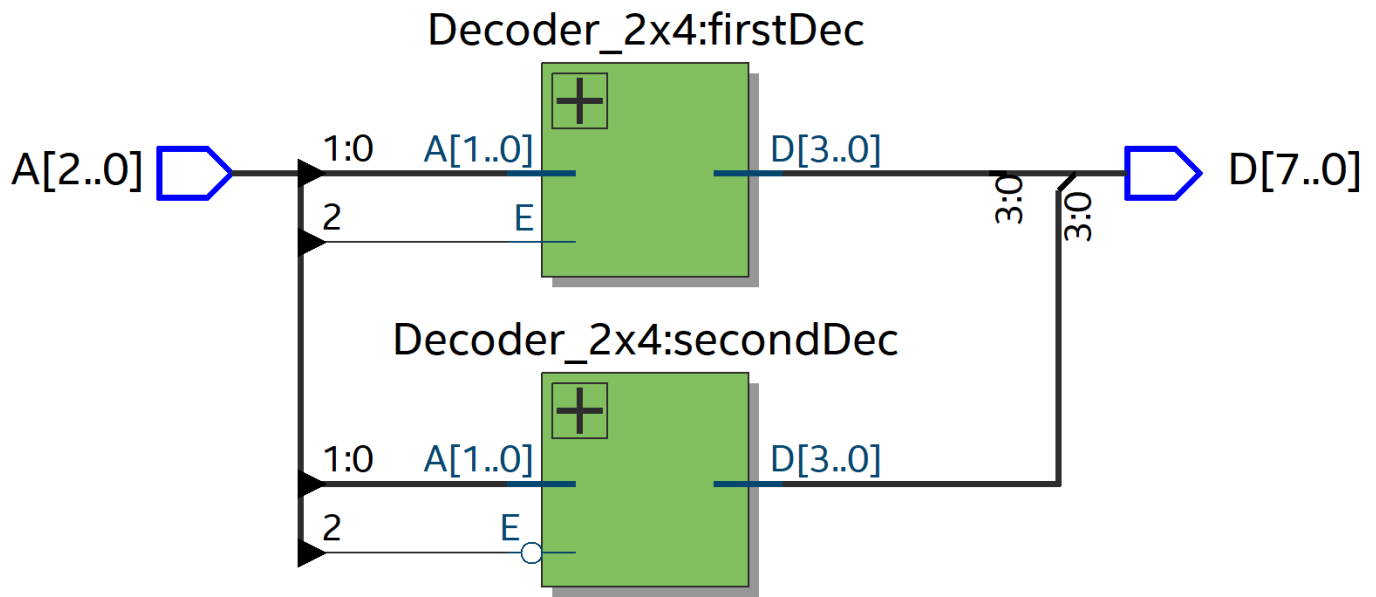


Figure 4: Internal Block Diagram of Decoder_3x8

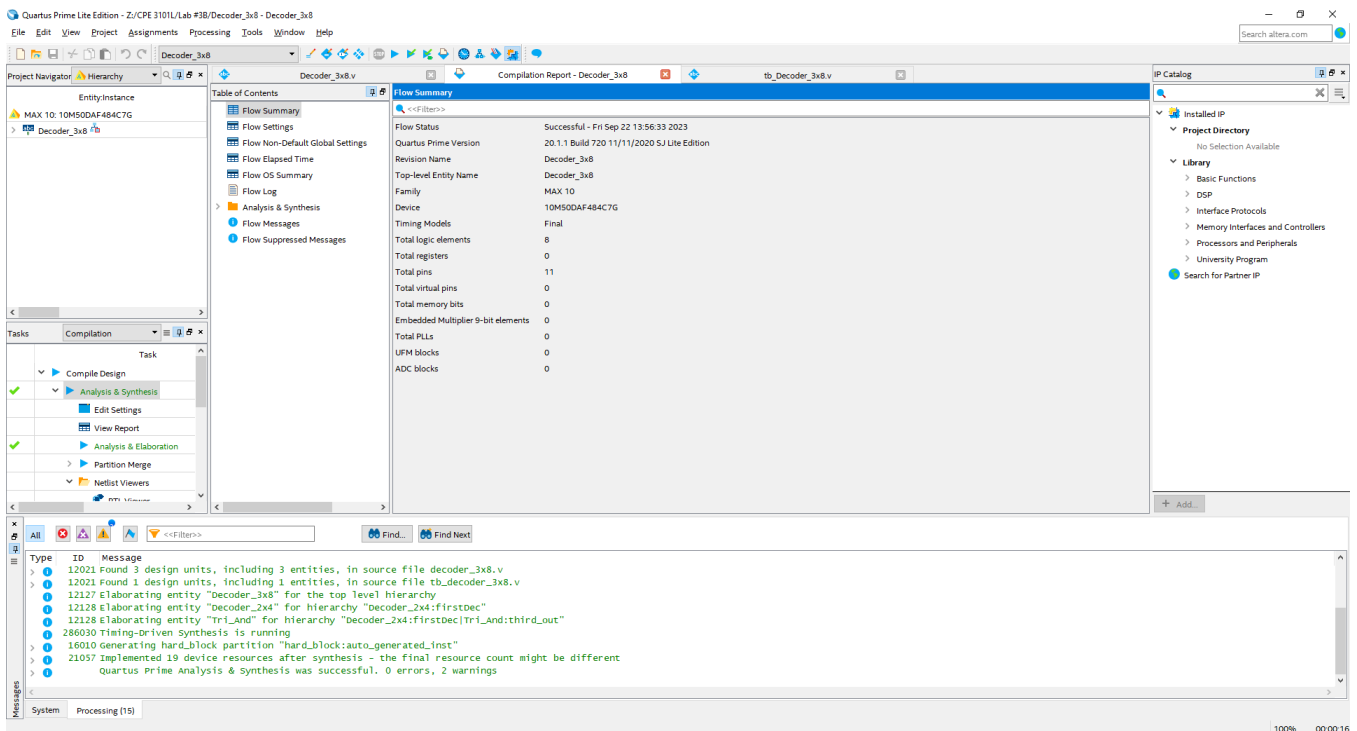


Figure 5: Successful Design Synthesis of Decoder_3x8

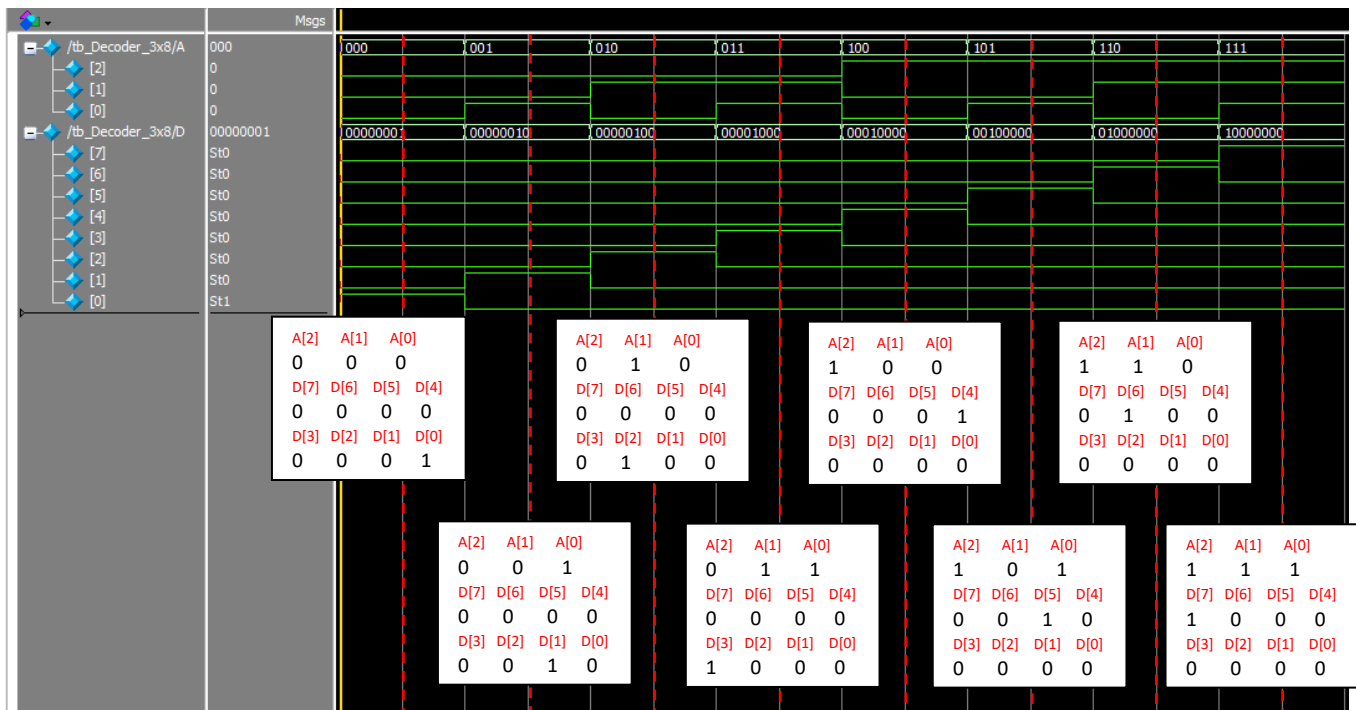


Figure 6: Successful Simulation Results of Decoder_3x8